

## 4.20 ELECTRICITY (448)

### 4.20.1 Electricity Paper 1 (448/1)

#### SECTION A

1. (a) **Procedure of connecting an ammeter to take measurements in a circuit**

- Turn - off the power
- Ammeter should be connected in series with the load current.
- Observe polarity.
- Select the range starting from the highest.

(4 ×  $\frac{1}{2}$  = 2 marks)

(b) (i) **Nominal resistance**

$$\begin{array}{cccccc} \text{Orange} & & \text{Black} & & \text{Brown} & \\ 3 & & 0 & \times & 10^1 & = 300 \Omega \end{array}$$

∴ Nominal = 300 Ω (1 mark)

(ii) **Maximum resistance**

$$300 + 5\% = 315 \Omega \quad (2 \text{ marks})$$

2. (a) **Circuit diagram**

- Shows connection of every component.
- Shows values of components.
- Shows the position of the components.
- Shows functionality of the circuit.

(any 2 × 1 = 2 marks)

(b) **Bills of materials**

- Materials/parts.
- Quantity.
- Size.
- Estimate costs.

(4 ×  $\frac{1}{2}$  = 2 marks)

3. (a) (i) **Forward bias**

reduces ( $\frac{1}{2}$ ) the PN-junction (depletion layer) and hence the diode conducts ( $\frac{1}{2}$ ).

(ii) **Reverse bias**

increases ( $\frac{1}{2}$ ) the PN-junction (depletion layer) hence the diode does not conduct ( $\frac{1}{2}$ ).

(2 marks)


- (b) (i)  $I_{F(\max)}$ : is the maximum forward current that the diode can pass without burning out. (1 mark)
- (ii)  $V_{F(\text{typ})}$ : is the forward voltage across the diode at the typical operating current. (1 mark)

4. (a)  $I_p = \frac{V}{R}$   $(\frac{1}{2})$   
 $= \frac{100 \text{ V}_{\text{rms}}}{1 \text{ k}\Omega}$   $(\frac{1}{2})$   
 $= 0.1 \text{ A}$   $(\frac{1}{2})$

(b)  $N_1 I_1 = N_2 I_2$  (1)  
 $\therefore 1200 \times 0.1 = 400 \times I_2$   $(\frac{1}{2})$   
 $I_2 = \frac{120}{400} = 0.3 \text{ A}$   $(\frac{1}{2})$   
 $V_2 = I_2 R_2$   $(\frac{1}{2})$   
 $= 0.3 \times 8000$   $(\frac{1}{2})$   
 $= 2,400$   $(\frac{1}{2})$


(5 marks)

5. (a)

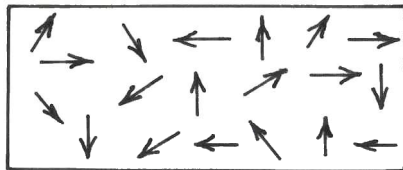

Drawing =  $(\frac{1}{2})$   
 Labelling =  $(\frac{1}{2})$   
 Direction =  $(\frac{1}{2})$   
 =  $1(\frac{1}{2})$  marks

(b)

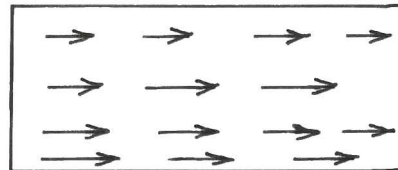

Drawing =  $(\frac{1}{2})$   
 Labelling =  $(\frac{1}{2})$   
 Direction =  $(\frac{1}{2})$   
 =  $1(\frac{1}{2})$  marks

6. (a) (i)  $E = 5 + (I \times R_1)$   $(\frac{1}{2})$   
 $= 5 + (2 \times 10^{-3} \times 2000)$   $(\frac{1}{2})$   
 $= 5 + 4$   
 $= 9 \text{ V}$   $(\frac{1}{2})$

$$(ii) \quad R_2 = \frac{V_2}{I} \quad \left(\frac{1}{2}\right) = \frac{4V}{2mA} \quad \left(\frac{1}{2}\right) = 2 \text{ k}\Omega \quad \left(\frac{1}{2}\right)$$

$$(iii) \quad R_3 = \frac{V_3}{I} = \frac{1V}{2mA} = 0.5 \text{ k} \quad (1)$$

(4 marks)

(b) (i) **Energy consumed**

$$\text{Lights } 5 \times 60 \times 4 = 1.2 \text{ kwh} \quad \left(\frac{1}{2}\right)$$

$$\text{Kettle } 1 \times 2 \times 0.5 = 1.0 \text{ kwh} \quad \left(\frac{1}{2}\right)$$

$$\text{Total energy} = 2.2 \text{ kwh} \quad (1)$$

(ii) **Cost of energy**

$$= 2.2 \times 80 = 1.76 \text{ sh} \quad (1)$$

(3 marks)

7. (a) **Safety precautions to be observed**

- Ensure that the equipment is properly earthed.
- Do not use it in damp areas.
- Always remove the plug from the socket when the equipment is not in use.
- When using extensions, ensure the joints are firm and insulated using the electricians insulation tape.
- Hold it firmly.
- Avoid loose clothing like ties.

(any 3 × 1 = 3 marks)

(b) **Communication service providers in Kenya**

- Telkom Kenya
- Safaricom
- Airtel
- Yu

(4 ×  $\frac{1}{2}$  = 2 marks)  
or any other existing ones

8. (a) **Insulating materials used in electrical circuits**

- PVC
- Porcelain
- Magnesium oxide
- Paper
- Rubber
- Air
- Formica

(4 ×  $\frac{1}{2}$  = 2 marks)

(b) **Advantages of PVC**

- Easy of erection.
- It is cheap.
- It is resistant to corrosion.
- It is light.
- There is no risk to earth leaks.

(any 3 × 1 = 3 marks)

9. (a) **Inductance required**

$$L = \frac{1}{4\pi^2 f^2 C} \quad \left(\frac{1}{2}\right)$$

$$= \frac{1}{4\pi^2 (1.5 \times 10^5)^2 (10^{-12})} \quad \left(\frac{1}{2}\right)$$

$$= 1.13 \times 10^{-3} \text{H} \quad 1$$

$$= 1.13 \text{ H}$$

(2 marks)

(b) (i) **Apparent power**

$$= IV \quad \left(\frac{1}{2}\right)$$

$$= 2.5 \times 240 \quad \left(\frac{1}{2}\right)$$

$$= 600 \text{ VA} \quad \left(\frac{1}{2}\right)$$

(ii) **True power**


$$= \text{apparent power} \times \text{power factor} \quad \left(\frac{1}{2}\right)$$

$$= 600 \times 0.6 \quad \left(\frac{1}{2}\right)$$

$$= 360 \text{ w} \quad \left(\frac{1}{2}\right)$$

(3 marks)

10.

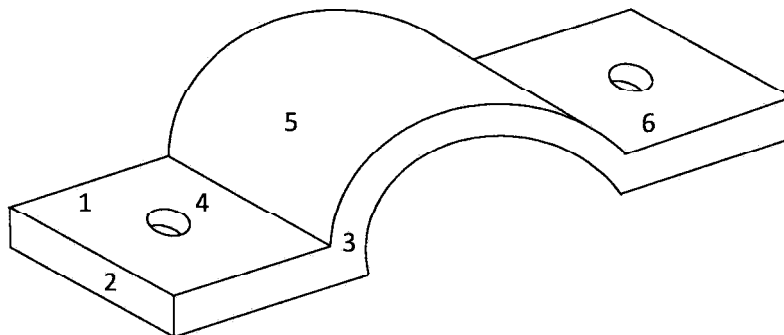


Faces	=	$4 \times \frac{1}{2} = 2$
Holes	=	$2 \times \frac{1}{2} = 1$
Projection	=	1
Neatness	=	$\frac{1}{2}$
Proportionality	=	$\frac{1}{2}$

(5 marks)


SECTION B

11.

11.

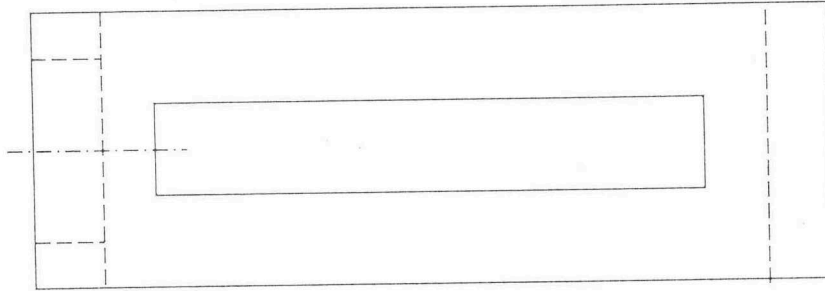

Complete Plan	
Faces=2×½	=1
Hidden details=2×1=2	<u>2</u>
TOTAL	<u>3</u>

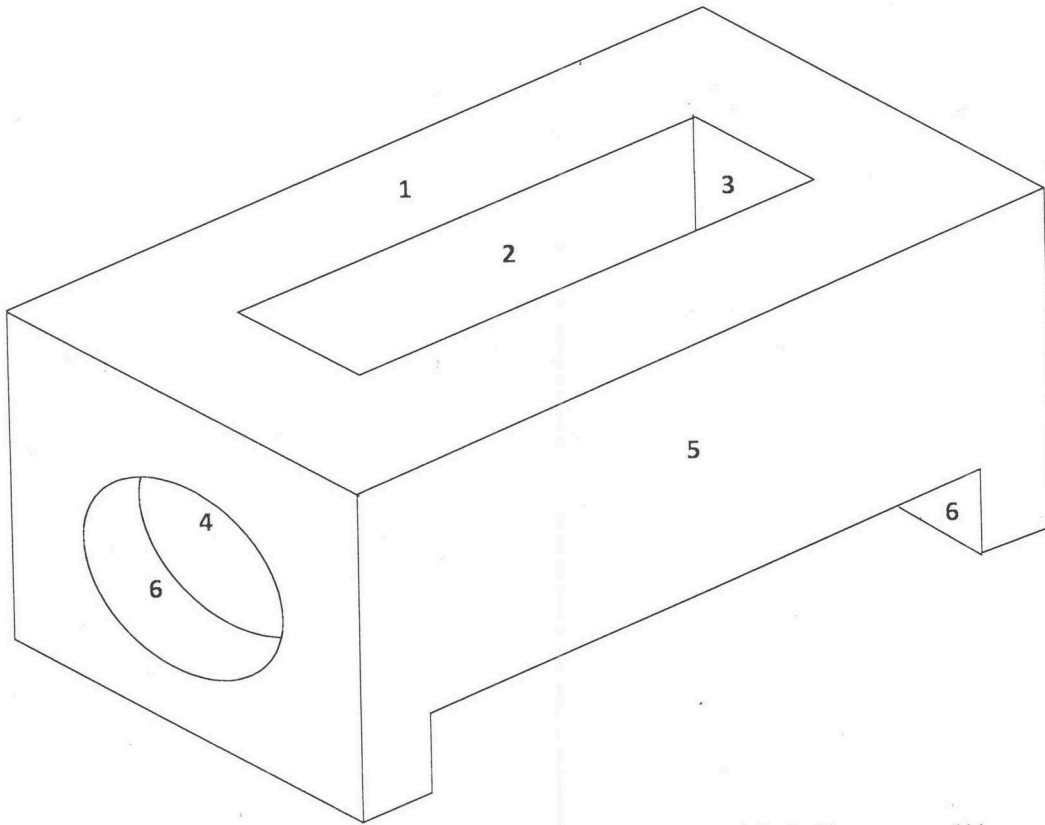

Faces 1, 5 and 7=3×½	=1½
Faces 2, 3,4,6 and 8=5×1	=5
Projection	=1
Placement of X	=½
Neatness	<u>½</u>
TOTAL	<u>9</u>

12. (a) **Name of waveforms**

A - sine wave  $(\frac{1}{2})$

B - saw tooth  $(\frac{1}{2})$

(b) **Number of cycles**

A - 2 cycles (1)

B -  $3\frac{1}{4}$  cycles (1)

(c) (i) **Frequency of waveform A**

$$= \frac{1}{T} \text{ where } T = \text{period} \quad (\frac{1}{2})$$

$$T = 50\mu \times 4 \quad (1)$$

$$= 200 \mu\text{s} \quad (1)$$

$$f = \frac{1}{T} = \frac{1}{200 \times 10^{-6}} = \frac{10^6}{200} \quad (\frac{1}{2})$$

$$= 5 \text{ kHz} \quad (1)$$

(ii) **Amplitude**

$$A = V_{\text{pk}} = 200 \text{ mV} \times 3 \quad (1)$$

$$= 600 \text{ mV} \quad (1)$$

$$= 0.6 \text{ V}$$

$$B = V_{\text{pk}} = 0.5 \text{ V} \times 2 \quad (1)$$

$$= 1 \text{ V}_{\text{pk}} \quad (1)$$

(iii) **RMS value of A**


$$= 0.707 \times V_{\text{pk}} \quad (1)$$

$$= 0.707 \times 0.6$$

$$= 0.424 \text{ V} \quad (1)$$

(13 marks)

13. (a)

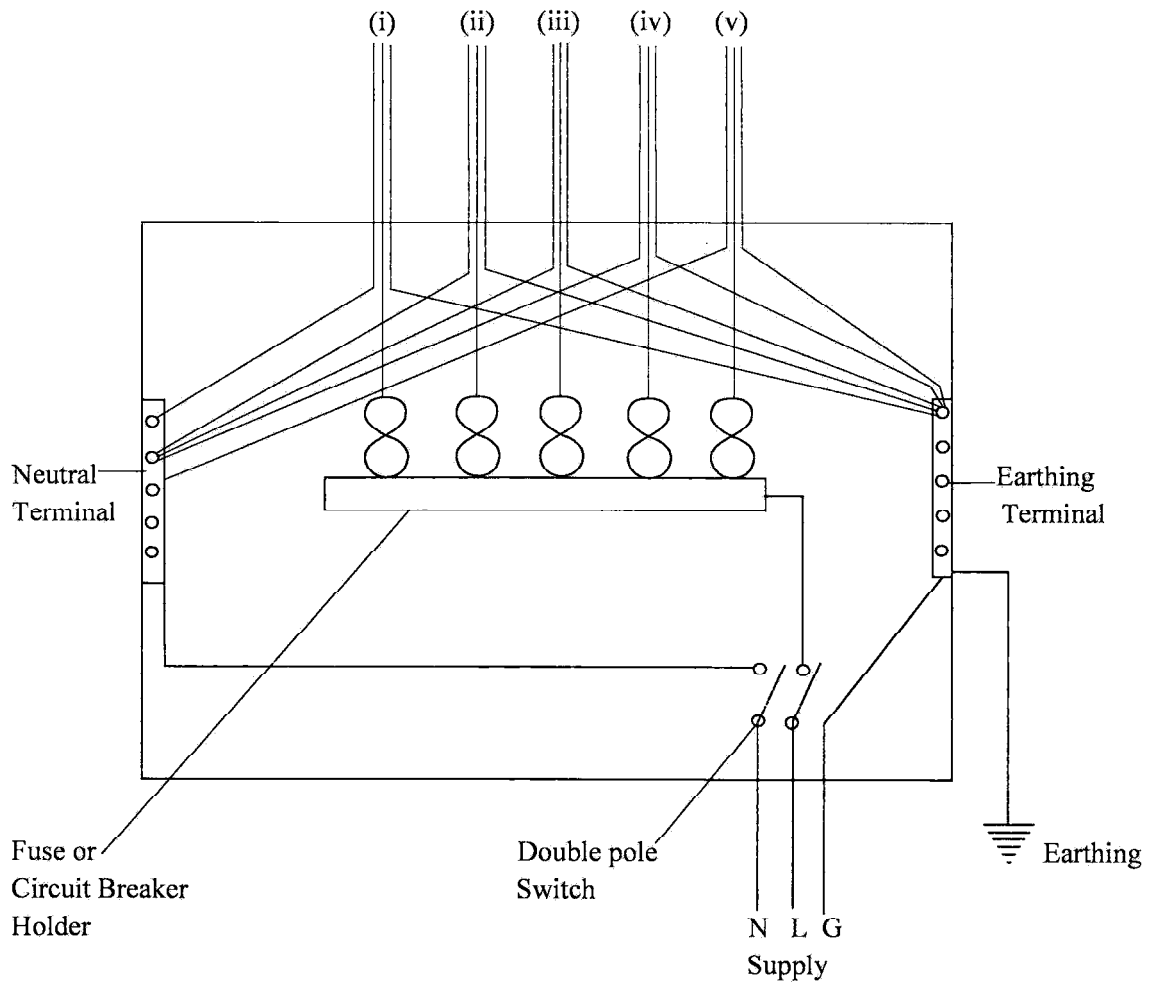

Correct Drawing = 8  
 Labelling 6 items = 3

(11 marks)

- (b)
- |       |                  |   |      |
|-------|------------------|---|------|
| (i)   | Lighting circuit | = | 5 A  |
| (ii)  | Ring circuit     | = | 30 A |
| (iii) | Water heater     | = | 20 A |
| (iv)  | Door bells       | = | 5 A  |
| (v)   | Cooker unit      | = | 45 A |

(any 4  $\times \frac{1}{2}$  = 2 marks)  
**(Total = 11 + 2 = 13 marks)**

14. (a) (i) **Type of transistor**  
NPN (1)

(ii) **Function of capacitor C**  
To block D.C (1)

(iii) **Type of biasing**  
Fixed bias (1)

(3 marks)

(b) (i)  $VR_1 = V_{CC} - V_{be}$  (1)

$$= 6.0 - 0.6$$

$$= 5.4 \text{ V} \quad (1)$$

(ii)  $I_B = \frac{VR_1}{R_1} = \frac{5.4}{100 \times 10^3}$  (1)

$$= 5.4 \times 10^{-5}$$

$$= 54 \mu\text{A}$$

(iii)  $I_C = \beta I_B$  (1)

$$= 54 \times 10^{-6} \times 50 \quad (1)$$

$$= 2.7 \text{ mA}$$

(iv) Voltage  $V_{CE}$

$$VR_2 = I_C \times R_2 \quad (1)$$

$$= 2.7 \text{ mA} \times 1 \times 10^3$$

$$= 2.7 \text{ V} \quad (1)$$

$$V_{CE} = V_{CC} - VR_2 \quad (1)$$

$$= 6 - 2.7 \text{ V}$$

$$= 3.3 \text{ V} \quad (1)$$

(10 marks)



15. (a) (i)  $X_L = 2\pi fL$  (1)

$= 2\pi \times 50 \times 0.05$  ( $\frac{1}{2}$ )

$= 15.70 \Omega$  ( $\frac{1}{2}$ )

$X_C = \frac{1}{2\pi fc}$  (1)

$= \frac{1}{2\pi \times 50 \times 2 \times 10^{-6}}$  ( $\frac{1}{2}$ )

$= 1592 \Omega$  ( $\frac{1}{2}$ )

$Z = \sqrt{R^2 + (X_C - X_L)^2}$  (1)

$= \sqrt{1000^2 + (1592 - 15.7)^2}$  (1)

$= 1866 \Omega$  (1)

(7 marks)


(ii) Current =  $\frac{V}{Z}$  (1)

$= \frac{240}{1866}$  (1)

$= 0.12 \text{ A}$  ( $\frac{1}{2}$ )    Amps ( $\frac{1}{2}$ ) (1)

(3 marks)

(b)

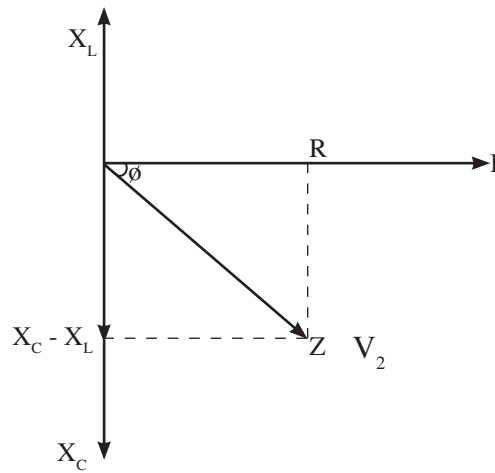

Axes = 1  
 Labelling =  $4 \times \frac{1}{2} = 2$

(3 marks)